

## Characteristics of BJT-2

### Output Characteristics for Common Emitter configuration:

The output characteristic for transistor is a graph between output current and output voltage on the basis of different input current. In common Emitter configuration the output current is  $I_C$  and output voltage is  $V_{CE}$  and input current is  $I_B$ . So output characteristics for common emitter will be a graph between  $I_C$  and  $V_{CE}$  on the basis of different values of  $I_B$ .

For pnp transistor to work in active region emitter junction should be forward bias and collector junction should be reverse bias. For emitter junction forward bias  $V_{BE}$  should be negative, and to make collector junction reverse biased the voltage  $V_{CB}$  should be negative as well as greater than  $V_{BE}$  in magnitude i.e.  $|V_{CB}| > |V_{BE}|$ .

Here we have to apply  $V_{BE}$  in input side and  $V_{CE}$  on output side. On applying KVL between terminals of BJT we can find relation between voltages.

$$V_{BE} + V_{CB} - V_{CE} = 0 \Rightarrow V_{CE} = V_{CB} + V_{BE}$$

From equation  $V_{CE} = V_{CB} + V_{BE}$ , we can see that, if  $V_{BE}$  is negative (to make emitter junction of pnp forward bias) then to reverse bias the collector junction of pnp transistor  $V_{CE}$  should be negative.

Suppose for Si (pnp) transistor,  $V_{BE} = -0.7V$ , then to make  $V_{CB}$  negative and greater than  $V_{BE}$  (i.e. 0.7 v) the  $V_{CE}$  should be at least greater than 1.4 in magnitude and with negative sign. i.e.  $V_{CE} = -1.42$  or

$$|V_{CE}| > 1.4$$

Means  $V_{CE}$  can be  $-1.41, -1.42, \dots, -1.5$  and so on

**Therefore we can say that to make pnp (Si transistor) in active region  $V_{CE}$  should be negative and greater than 1.4V in magnitude.**

Similarly to make a Si (pnp transistor) in saturation region the emitter junction and collector junction both should be forward bias. Means  $V_{BE}$  should be negative and to make  $V_{CB}$  positive and smaller in magnitude than  $V_{BE}$  (i.e.  $|V_{CB}| < |V_{BE}|$ ),  $V_{CE}$  should be always negative and lower than  $V_{BE}$  in magnitude.

Suppose  $V_{BE} = -0.7$  (for emitter junction Forward bias)

So for  $V_{CB} = +Ve$  and lower than  $V_{BE}$  in magnitude

$$\text{[From } V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = V_{BE} - V_{CE}$$

$$= -0.7 - V_{CE}] \quad V_{CE} \text{ can not be positive.}$$

That means for pnp transistor in common emitter case to be in saturation region  $V_{BE}$  should be negative and  $V_{CB}$  should be positive and lower than  $V_{BE}$  in magnitude. And to make this,  $V_{CE}$  will be always negative.

***So finally we can say to make a pnp transistor in active or saturation or in cut off  $V_{CE}$  will be always negative. Similarly for npn transistor it will be always positive.***

So to draw an output characteristics graph for pnp transistors between  $I_C$  and  $V_{CE}$  only negative values of  $V_{CE}$  will be used.

As we have discussed for pnp common emitter transistor  $I_C$  should be function of  $V_{CE}$  and  $I_B$  means

$$I_C = f(I_B, V_{CE}).$$

We know  $I_C = \alpha I_E + I_{CBO} (1 - e^{V_{CB} / \eta V_T})$  from common base configuration.

By using  $I_E = I_C + I_B$  and  $V_{CE} = V_{CB} + V_{BE}$

$$I_C = \alpha(I_C + I_B) + I_{CBO} (1 - e^{(V_{CE} - V_{BE}) / \eta V_T})$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO} (1 - e^{(V_{CE} - V_{BE}) / \eta V_T})$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO} (1 - e^{(V_{CE} - V_{BE}) / \eta V_T})$$

$$I_C = \beta I_B + (\beta + 1) I_{CBO} (1 - e^{(V_{CE} - V_{BE}) / \eta V_T})$$

Here we can see

$$I_C = f(I_B, V_{CE})$$

$$\beta = \frac{\alpha}{1 - \alpha}, \quad (\beta + 1) I_{CBO} = I_{CEO}$$

$I_{CEO}$  means current between collector and emitter when base is open.

So general equation of BJT in common emitter configuration will be

$$I_C = \beta I_B + I_{CEO} (1 - e^{(V_{CE} - V_{BE}) / \eta V_T}), \quad \text{This equation can be used to draw}$$

characteristics of BJT in common emitter configuration.

**Active Region:**

For active region emitter junction should be forward bias and collector junction should be reverse biased so  $\beta I_B$  will be present in the equation and  $e^{(V_{CE} - V_{BE}) / \eta V_T}$  will be neglected with respect to 1, and equation for active region will be

$$I_C = \beta I_B + I_{CEO}$$

So graph of  $I_C$  will be dependent on  $I_B$  and  $V_{CE}$  both, because on

$$V_{CE} \uparrow \Rightarrow V_{CB} \uparrow \Rightarrow \alpha \uparrow \Rightarrow \beta \uparrow \text{ (From base width modulation)}$$

(Means on increasing  $V_{CE} \Rightarrow \beta$  will be increased) and as we know  $\alpha$  varies from 0.92 to 0.99, for

$$\text{variation of } \alpha \text{ from 0.92 to 0.99, } \beta = \frac{0.92}{1-0.92} = \frac{0.92}{0.08} = 11.5, \beta = \frac{0.99}{1-0.99} = 99,$$

So for  $\alpha$  0.92 to 0.99,  $\beta$  varies from 11.5 to 99.

So variation in  $\beta$  with respect to  $V_{CE}$  is faster than variation in  $\alpha$ . So slope of graph in common emitter will be greater than common base in active region.


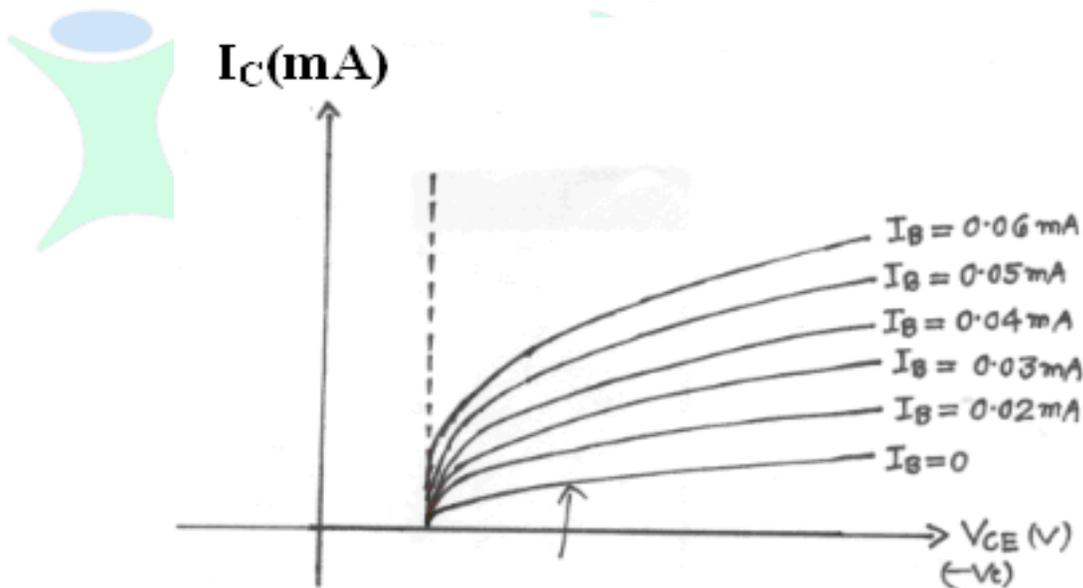


Figure-1(Active region)

### Saturation region:

For BJT to be in saturation region emitter junction should be forward bias and collector junction should also be forward biased. For PNP transistor  $V_{BE}$  and  $V_{CB}$  both should be negative and  $|V_{CB}| < |V_{BE}|$  is required for pnp in saturation region. For this  $V_{CE}$  will be always negative and

$|V_{CE}| < |V_{BE}|$ . Due to emitter junction forward bias  $\beta I_B$  will be available in the equation and  $e^{(V_{CE} - V_{BE})/\eta V_T}$  will be much greater than '1', so '1' will be neglected with respect to  $e^{(V_{CE} - V_{BE})/\eta V_T}$  and current equation for pnp transistor in saturation region will be  $I_C = \beta I_B + I_{CEO} (e^{(V_{CE} - V_{BE})/\eta V_T})$ . From this equation it is conform that variation in  $V_{CE}$  is dominating over variation in  $I_B$  on values of  $I_C$ . So  $I_C$  will be approximately dependent on  $V_{CE}$  exponentially and independent of  $I_B$  and  $I_E$ . That means  $I_C$  is saturated with respect to  $I_B$  so this region is called saturation region

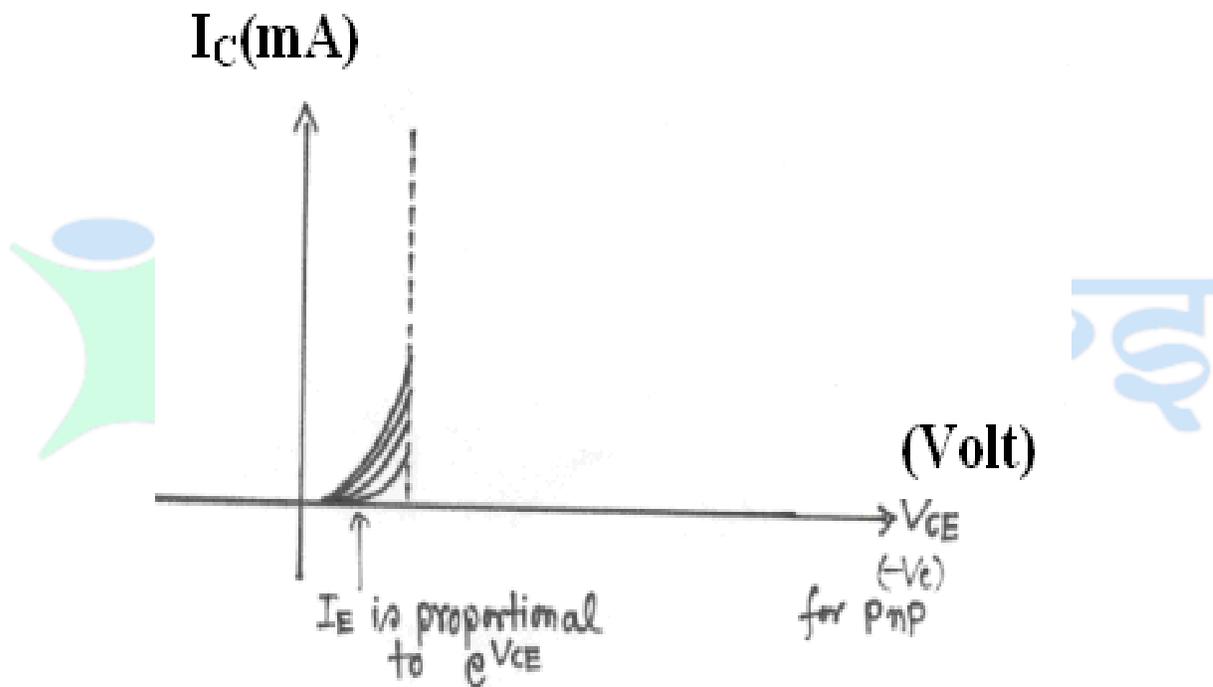

**Figure-2(Saturation region)**

Therefore we can say that in saturation region of output characteristics of common emitter configuration  $I_C$ , is saturated with respect to input current  $I_B$  and also  $I_E$ .

### **Cut off Region:**

In cut off region emitter junction is reverse biased and collector junction is also reverse biased. So  $V_{BE}$  and  $V_{CB}$  both should be applied in such a manner that can reverse bias the emitter junction and collector junction respectively. For pnp,  $V_{BE}$  should be positive and  $V_{CB}$  should be negative.

So in current equation

$I_B = 0$ , and  $e^{(V_{CE} - V_{BE}) / \eta V_T}$  will be neglected with respect to 1.

So current equation for cut off region will be

$$I_C = I_{CEO}$$

So we can say  $I_C$  is cut off from  $I_B$  &  $I_E$ , so this biasing condition will be called cut off region and graph will be as shown in figure-3.

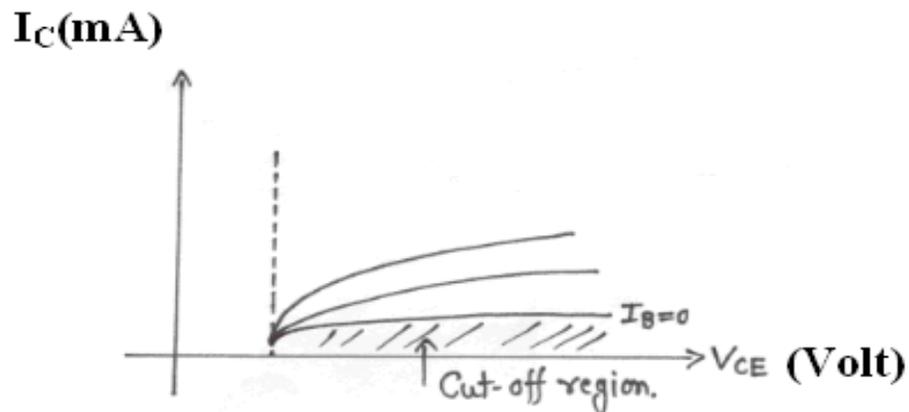


Figure-3(Cut off region)

From above discussion it is conform that output characteristics graph will be always for negative  $V_{CE}$  (for pnp). Active, saturation and cut off region will be on right side of vertical,  $I_C$ , axis. The slope of the graph will be greater than slope of graph in common base case. Means variation in  $I_C$  with respect  $V_{CE}$  will be greater than variation in  $I_C$  with respect  $V_{CB}$  (in common base) as shown in fig.

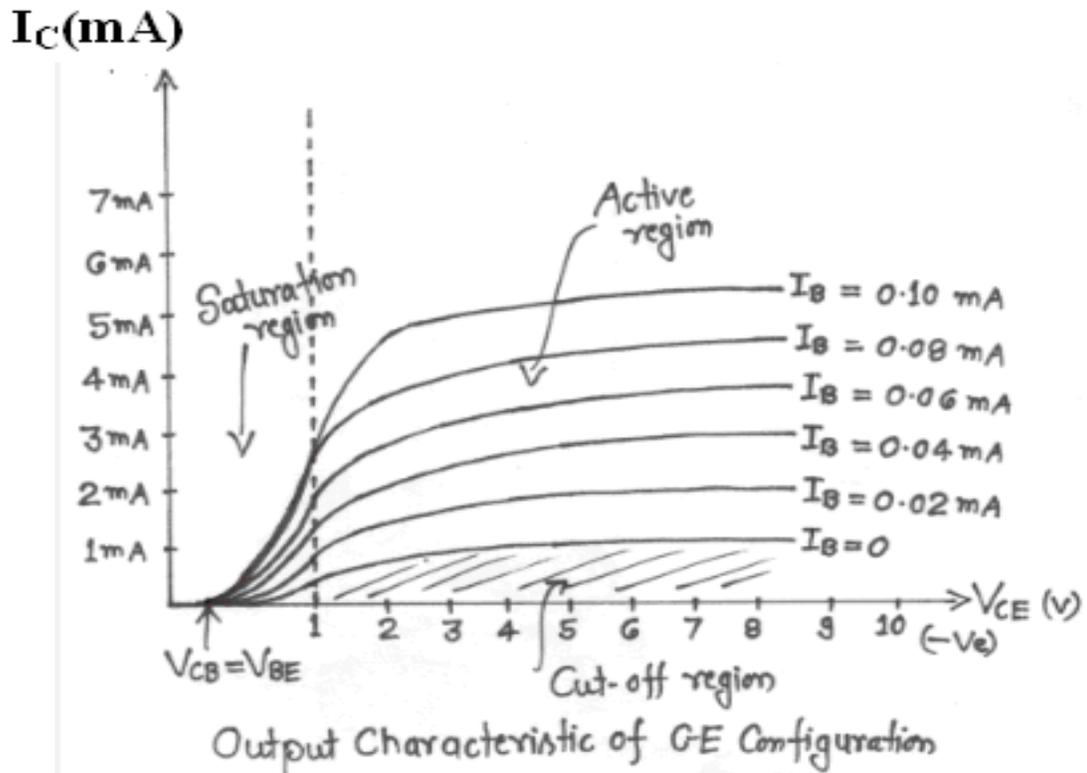


Figure-4 (Output characteristics of common emitter pnp transistor)